

Summer Science Project 3 Electronics

Using one of the following websites (you must indicate which one you used!!) create a working electronic circuit.

<http://www.kpsec.freeuk.com/proj.htm>

<http://www.knowledgehound.com/topics/electron.htm#clocks>

<http://library.thinkquest.org/16497/home/index.html>

Materials that you need for your project may be purchased from:

Radio Shack, a hobby shop or online. One site is:

<http://www.chaneyelectronics.com/>

Your final project must include:

1. The working circuit
2. A schematic diagram of your circuit
3. An explanation of the function of each component of your circuit